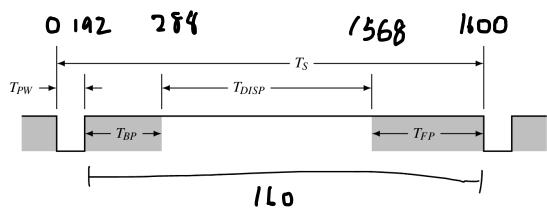



4 counters: 1 for row
1 for col
1 for vcount
1 for hcount

Following Design is
for VGA module

Hcount:



Vcount:

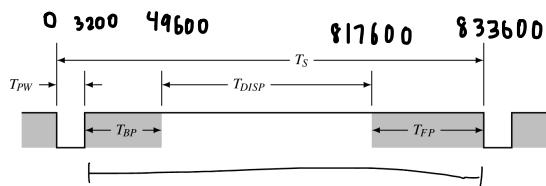

$$T_{disp} (vs) = 768000$$

$$T_s (hs) = 1600$$

$$768000 / 1600 = 480$$

There are 480 HS pulses during T_{disp} for VS.

480 rows

7 strips of board

6 tokens



each token is 45 pixels tall
each strip of board is 30 pixels tall

640 columns



7 tokens

8 strips of board

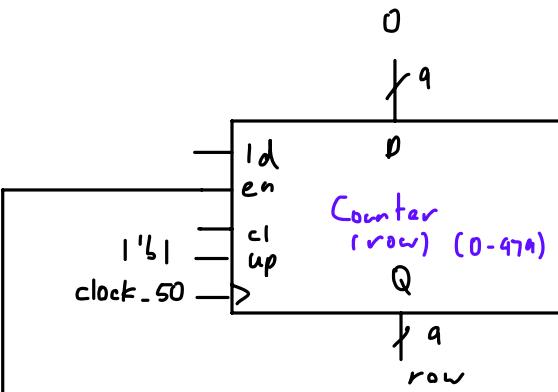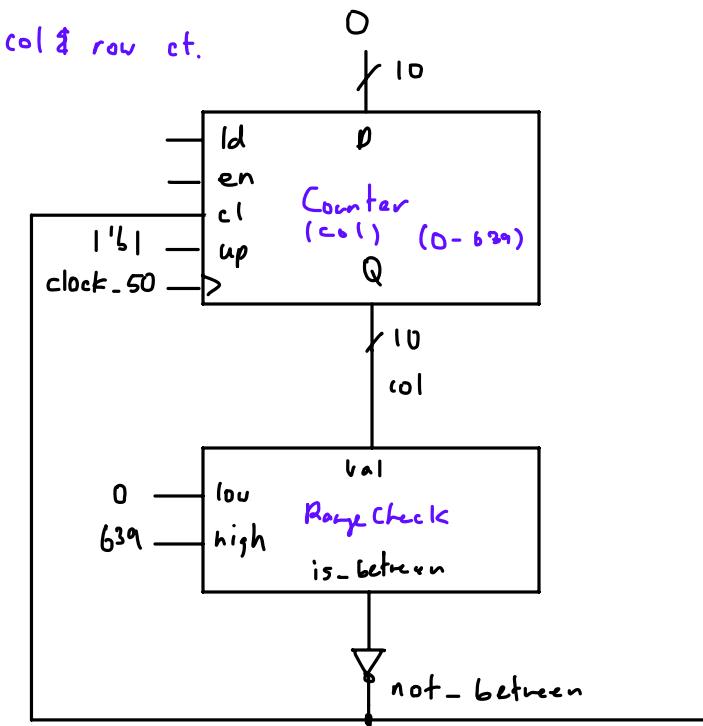
each token is 40 pixels wide
each strip of board is 45 pixels wide



H count

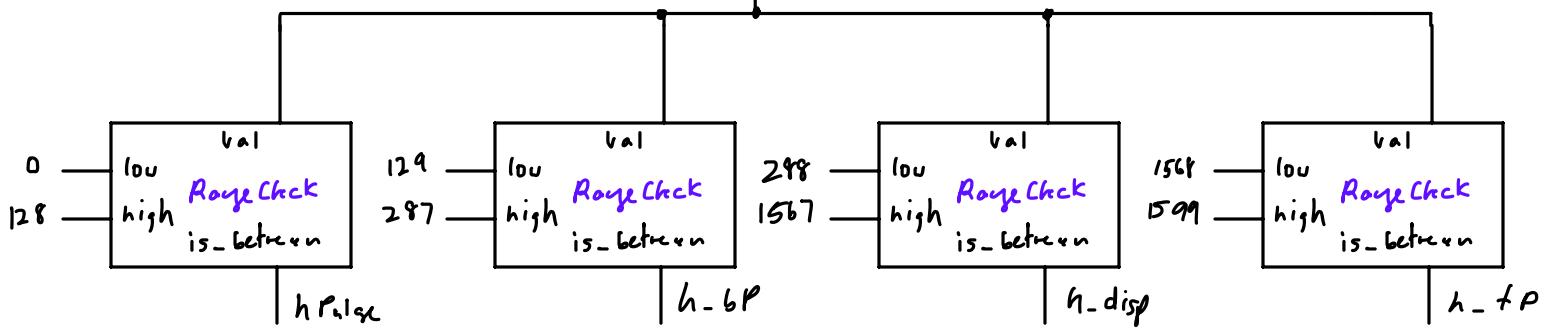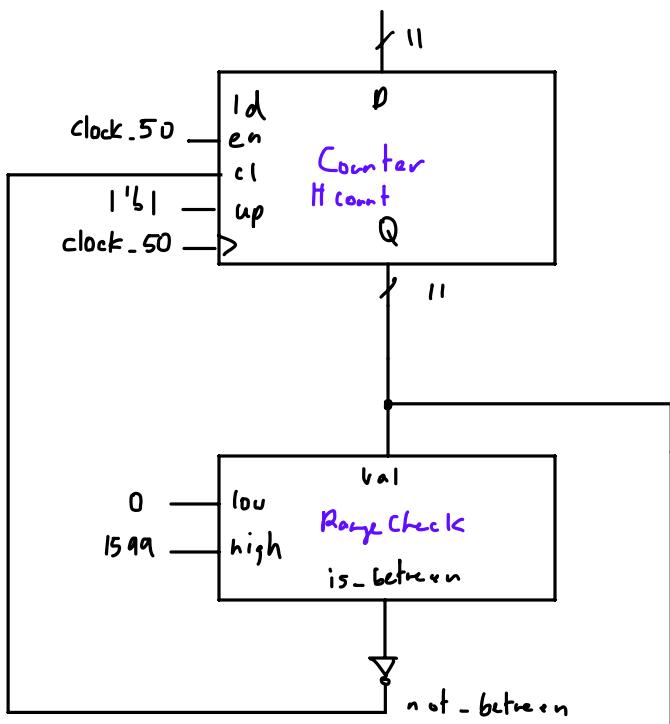


HCount & Row/Col count

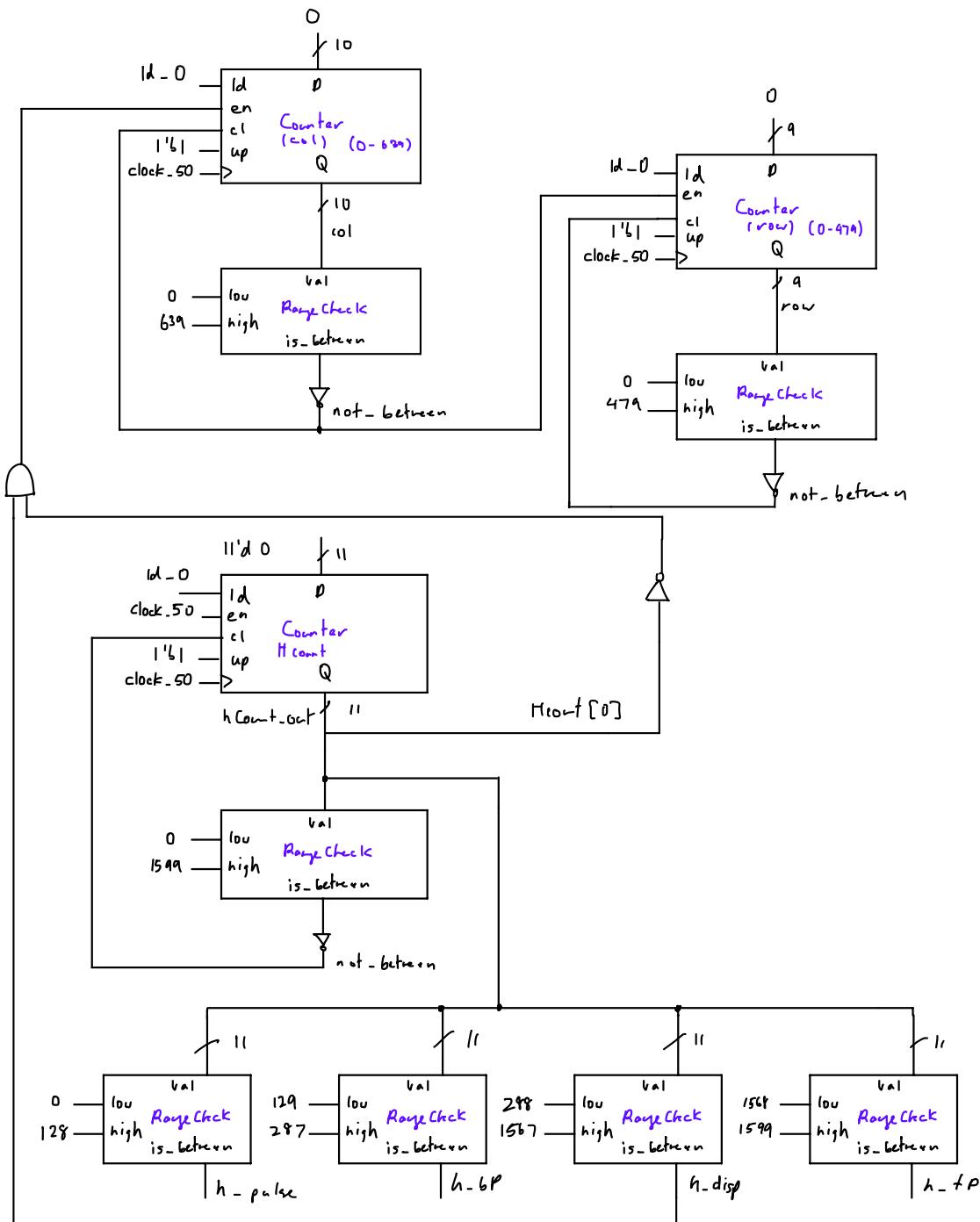


Vcount

20'd0

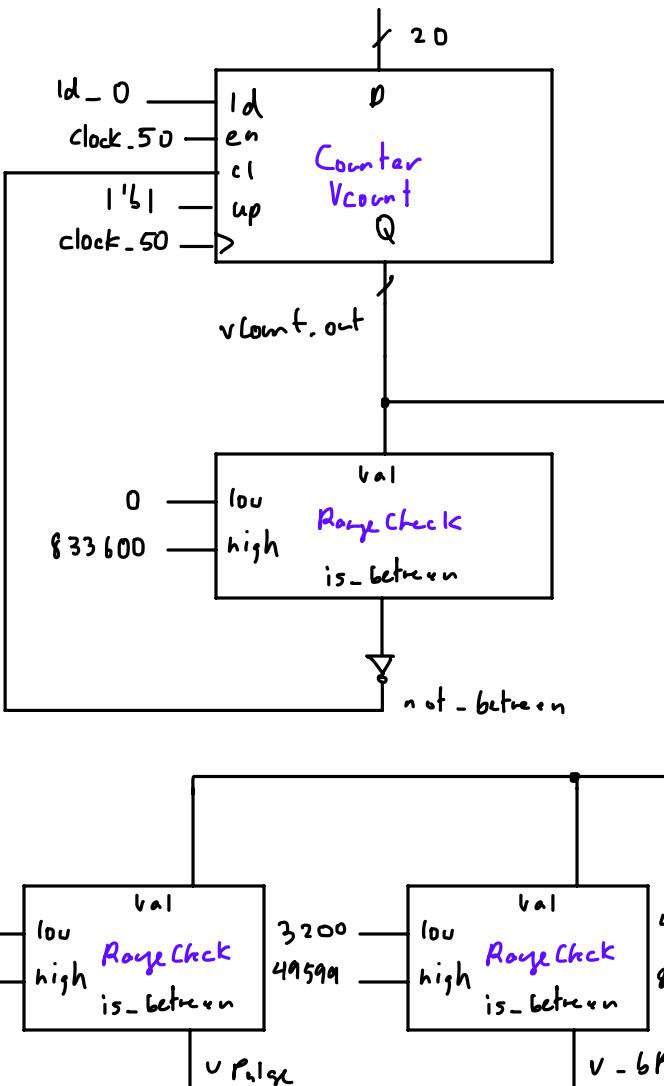




STD

Control points: **ld - 0**

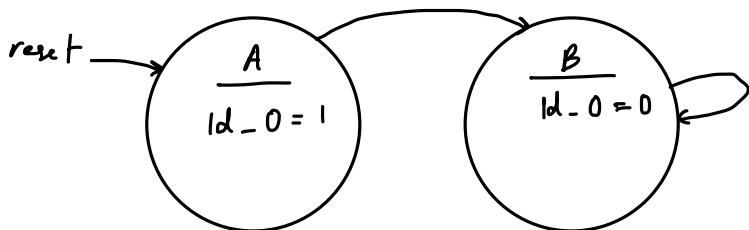


Board inputs row, col

output is_board

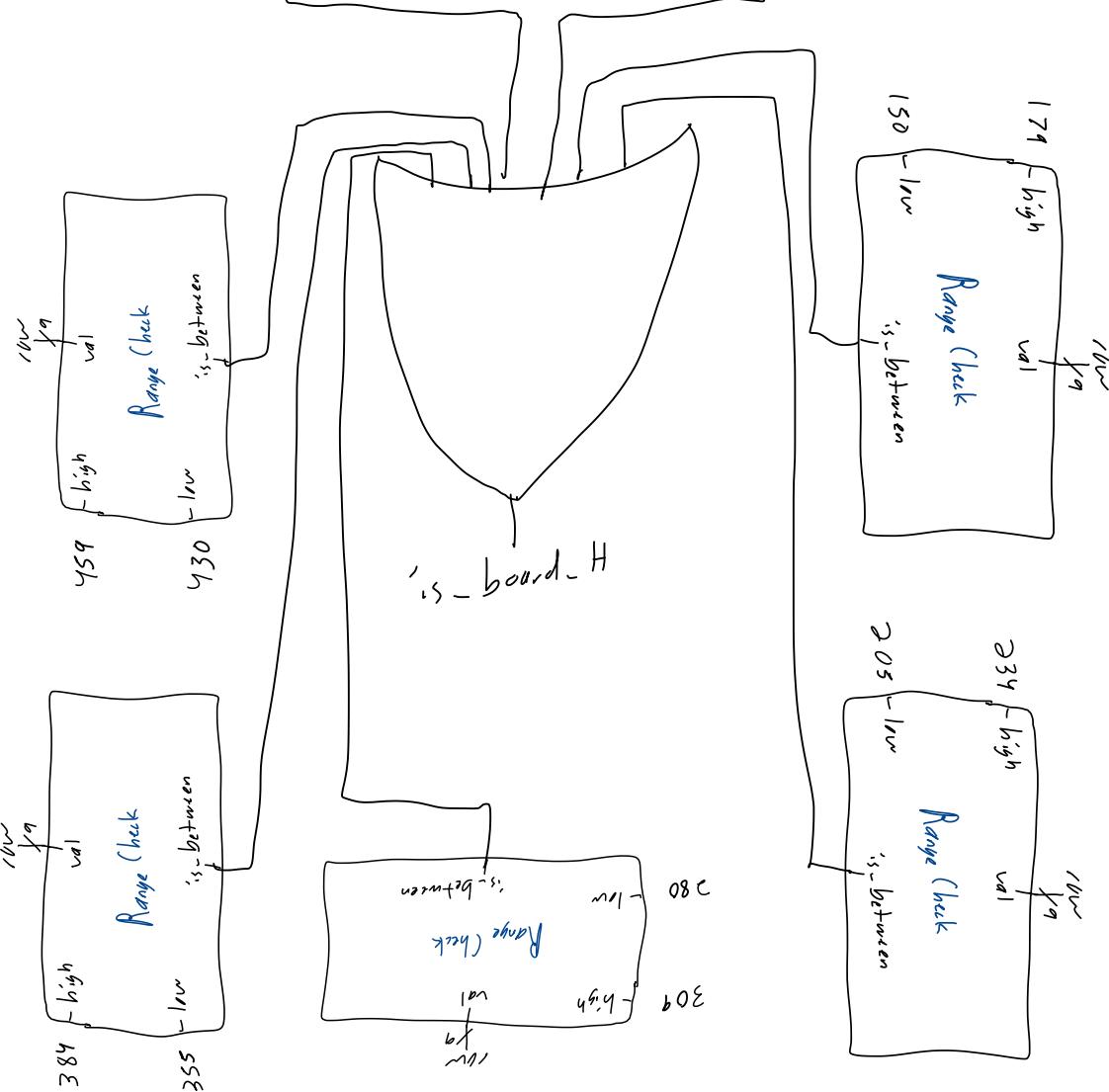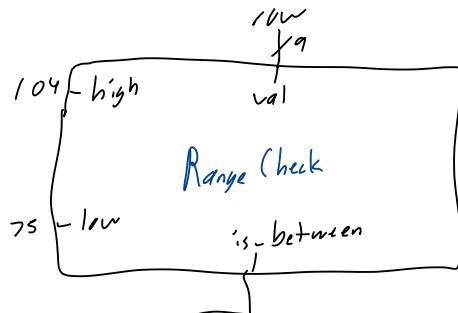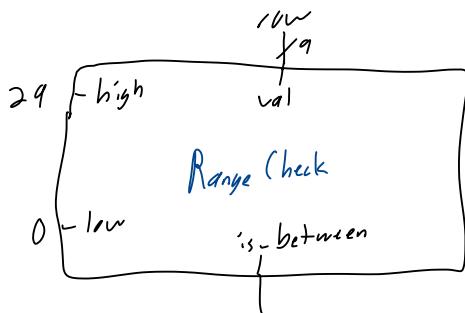




Board

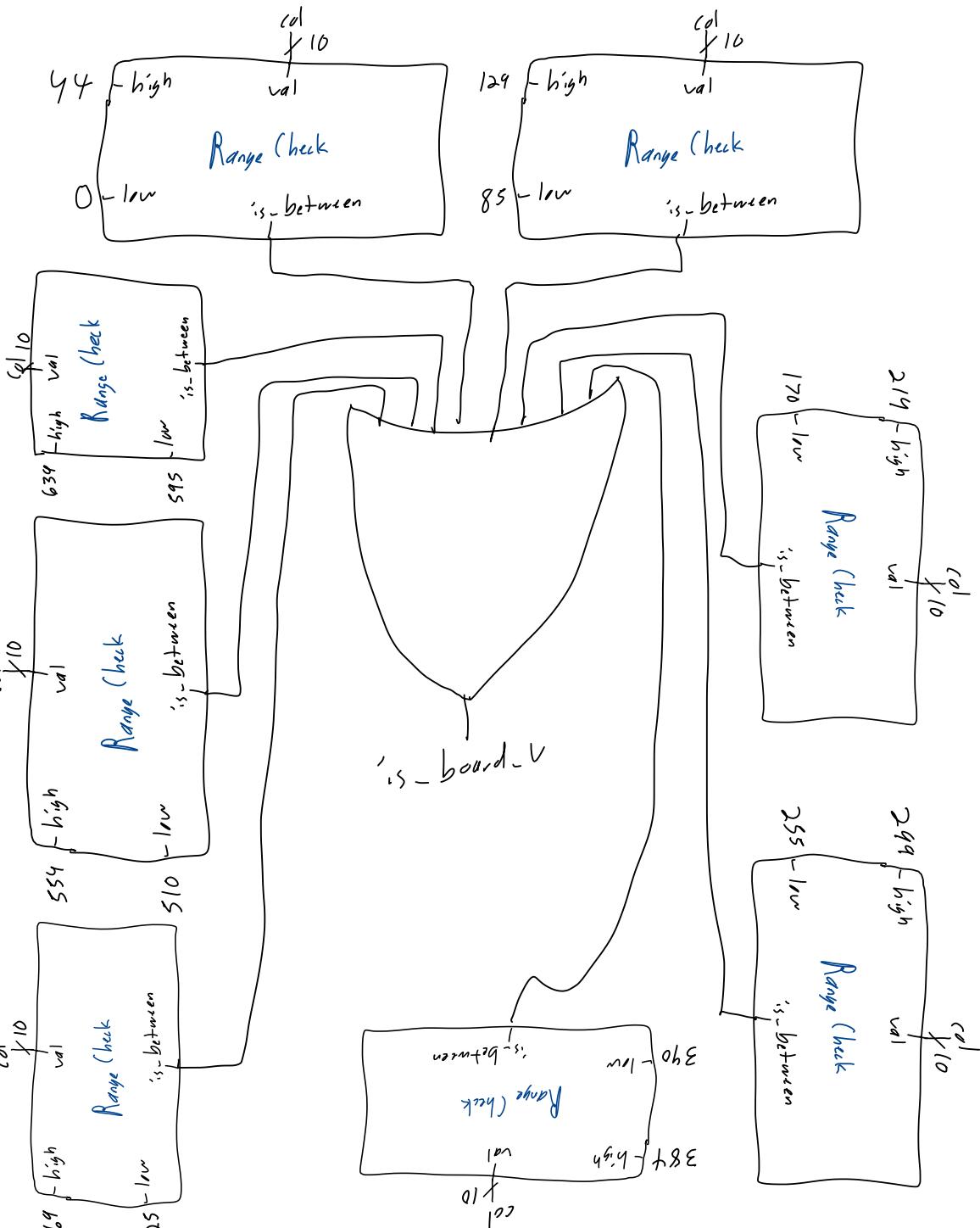




Board

$$\text{is_board} = \text{is_board_V} \mid \\ \text{is_board_H}$$


Taken inputs: row, col output: is-token

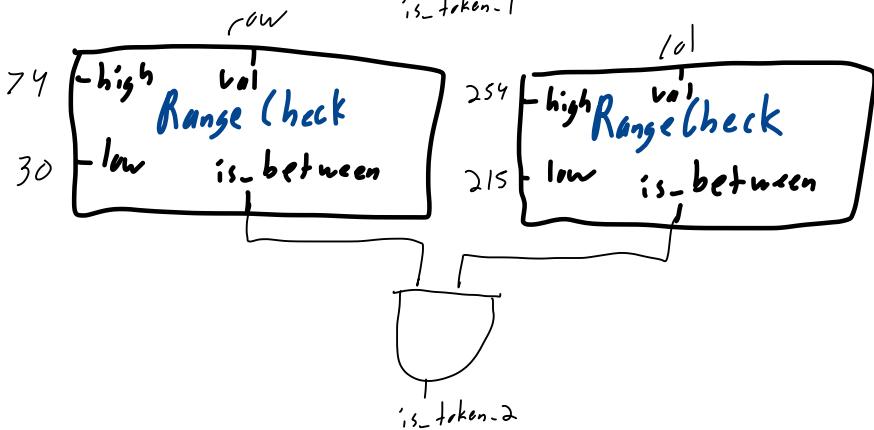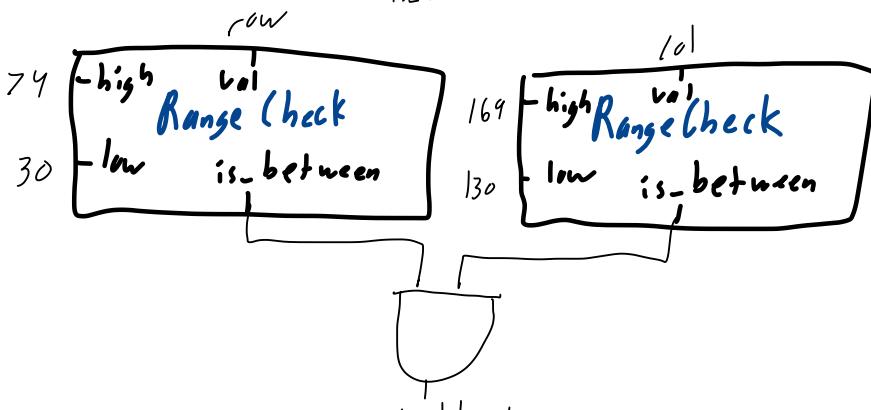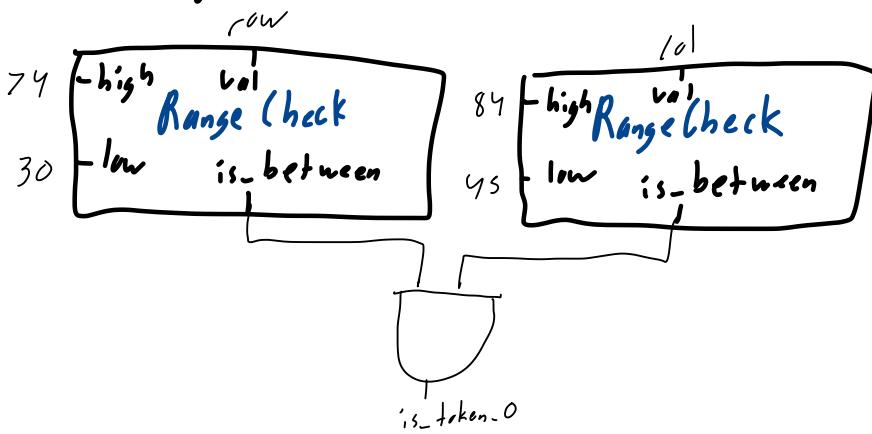

Token

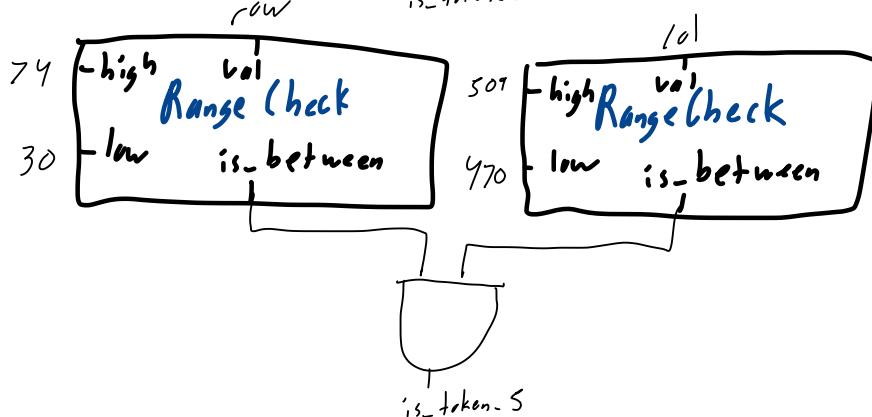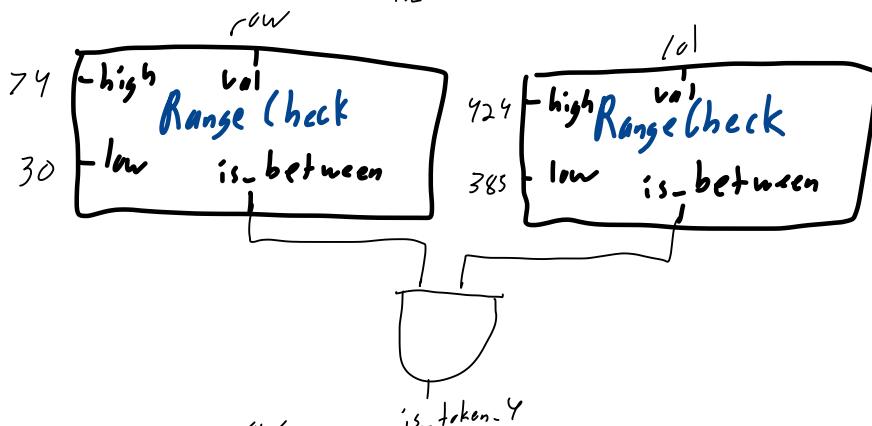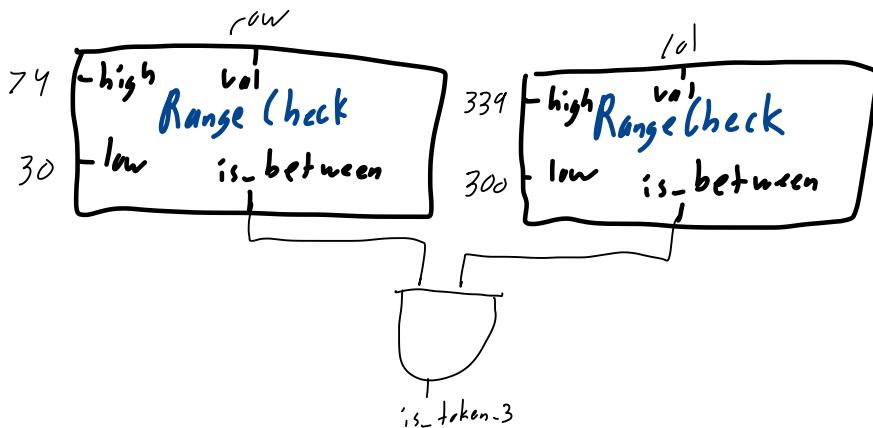


Token


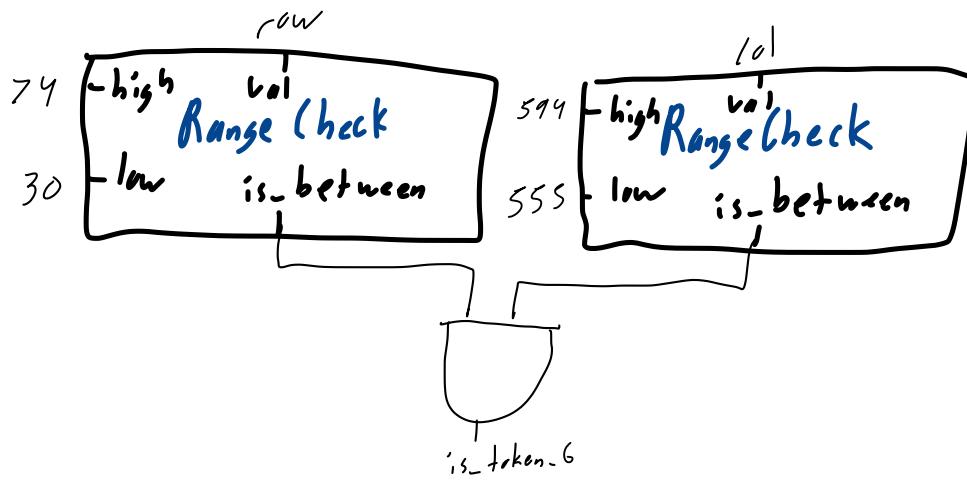


```
'is_token-row-0' = 'is_token_0 | is_token_1 |  
                     is_token_2 | is_token_3 |  
                     is_token_4 | is_token_5 |  
                     is_token_6'
```


Token

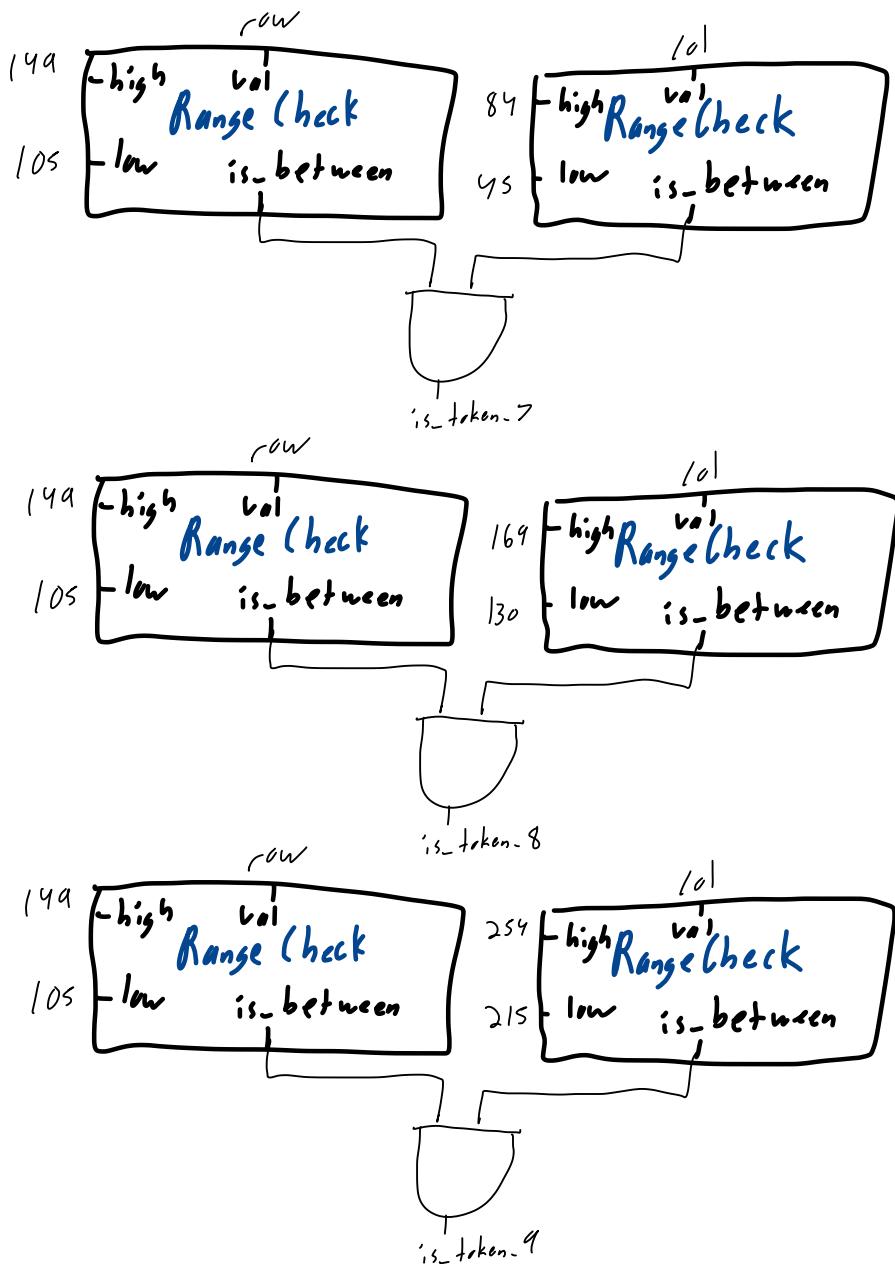

Tokens

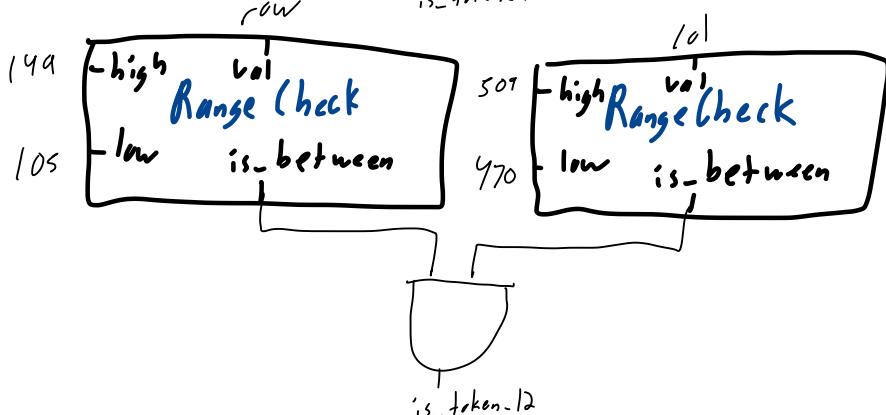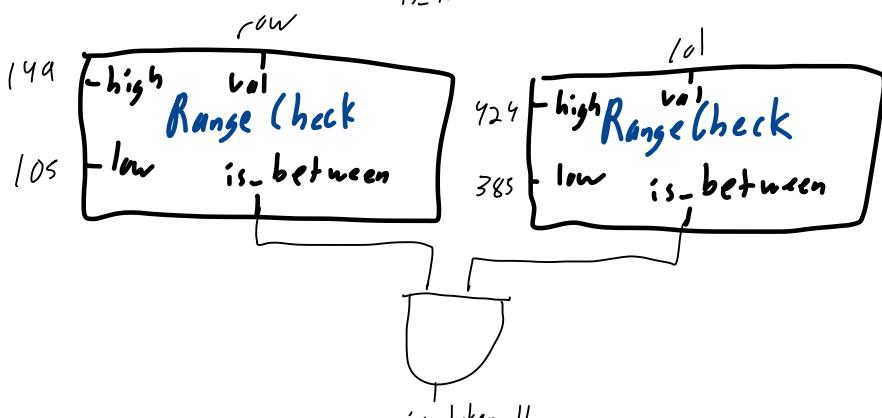


Token

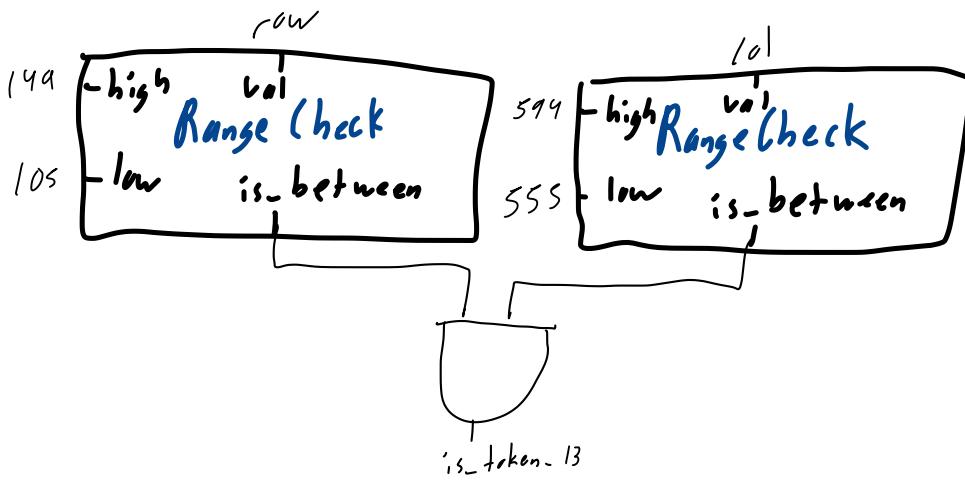


```
'is_token-row-1' = 'is_token_7' | 'is_token_8'  
                   'is_token_9' | 'is_token_10'  
                   'is_token_11' | 'is_token_12'  
                   'is_token_13'
```


Tcken

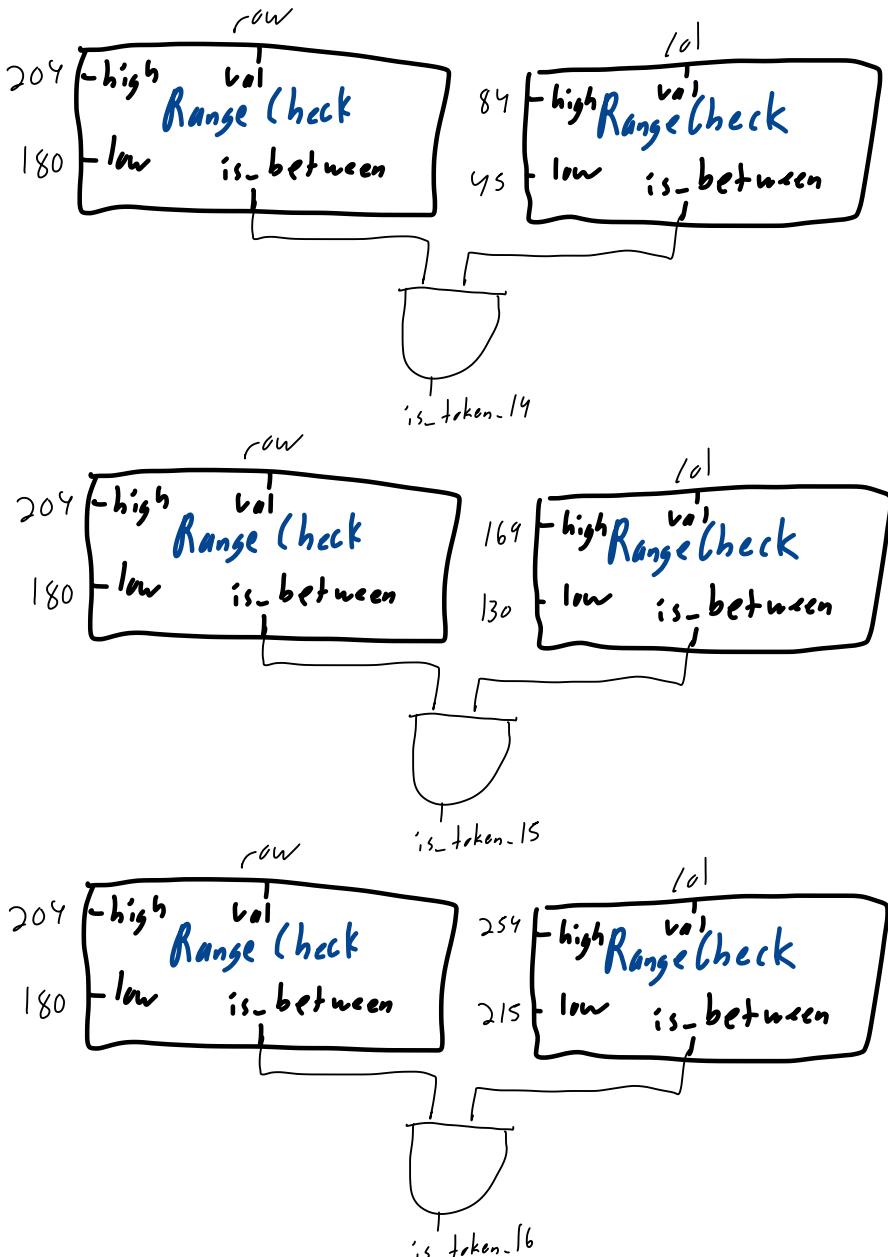


Tokens

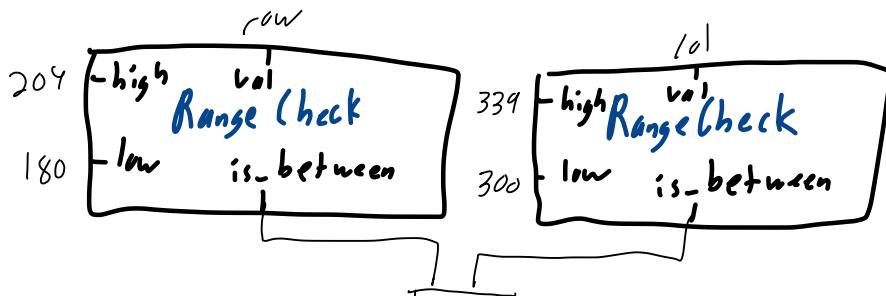


is_token-17

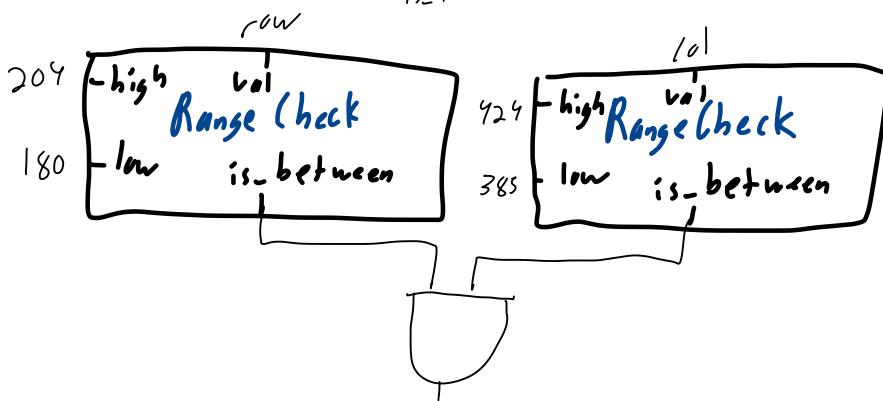

is_token-18

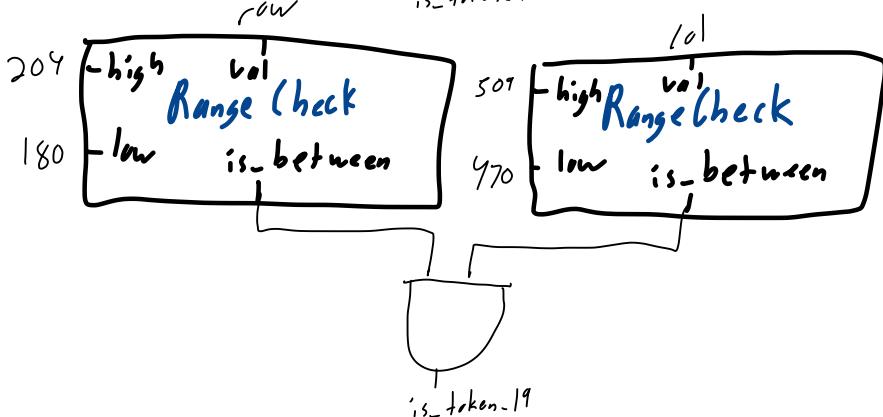


is_token-19



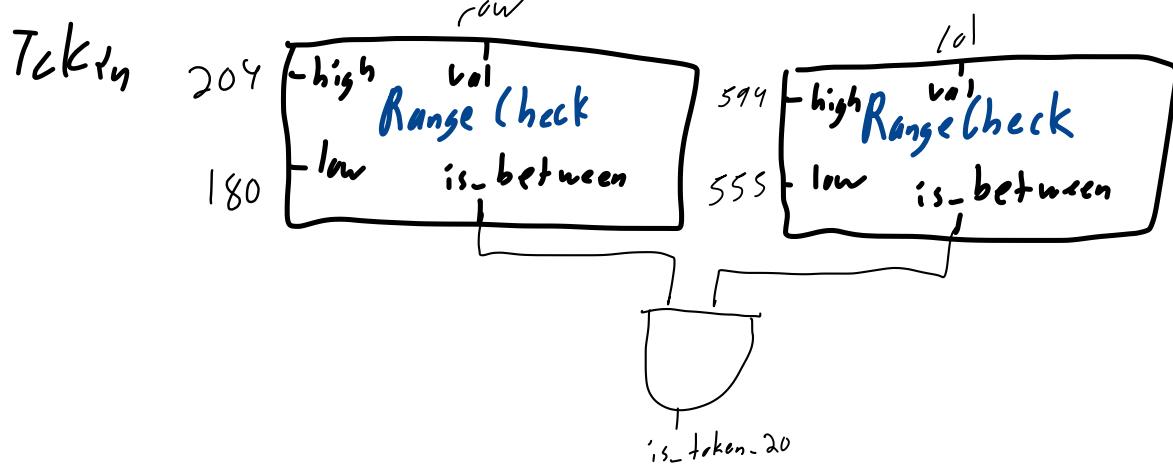


`'is_token-row-2' = 'is_token_14 | is_token_15 |
 'is_token_16 | is_token_17 |
 'is_token_18 | is_token_19 |
 'is_token_20'`


Token

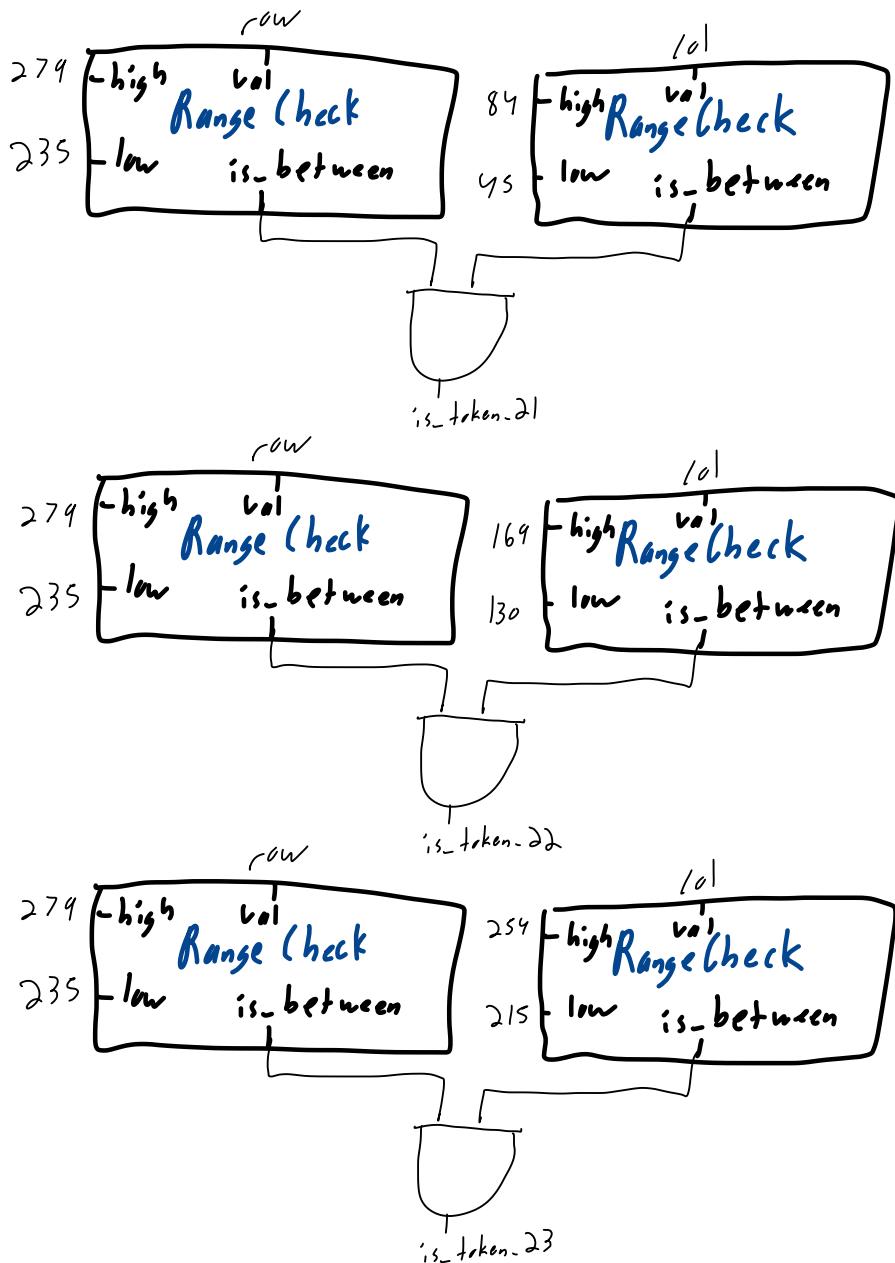

Token

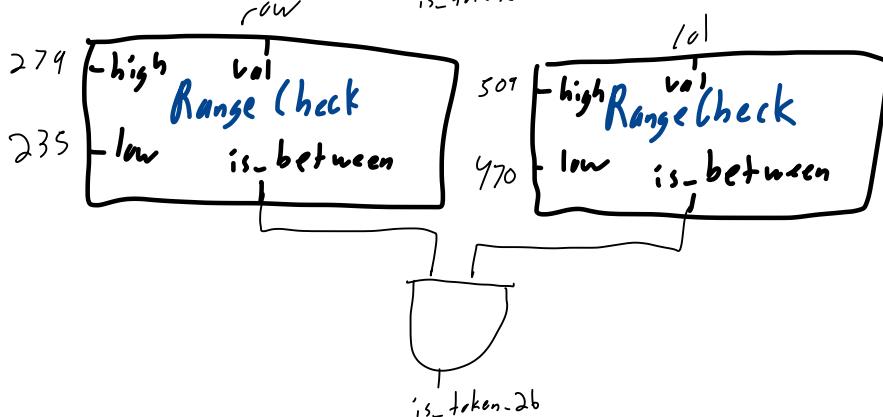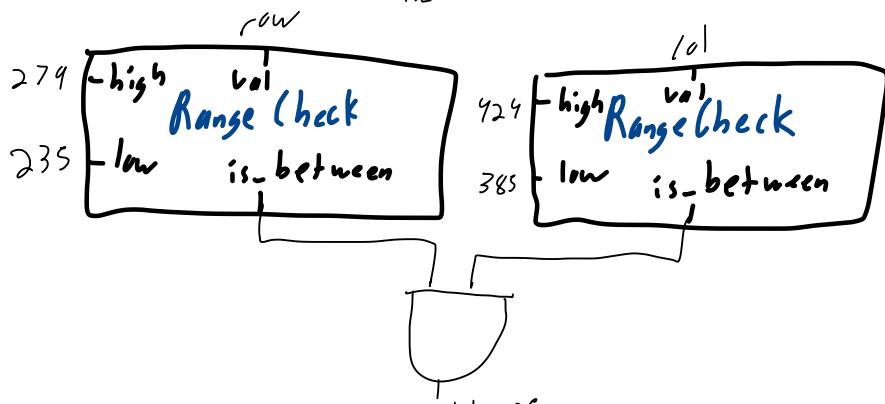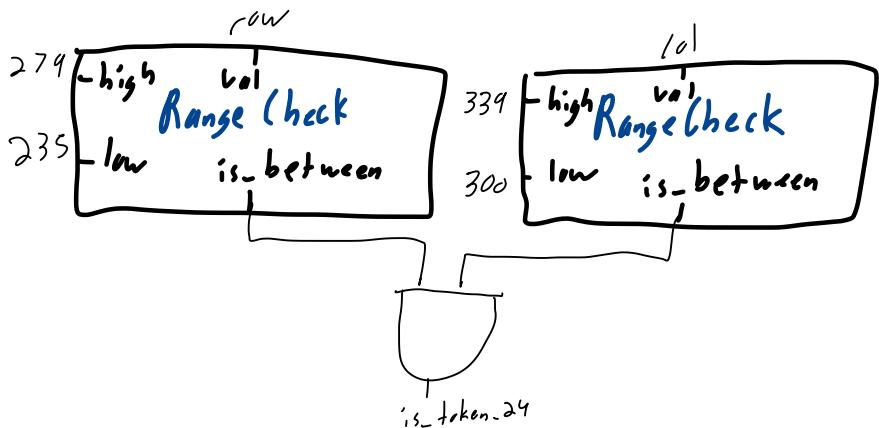


Token



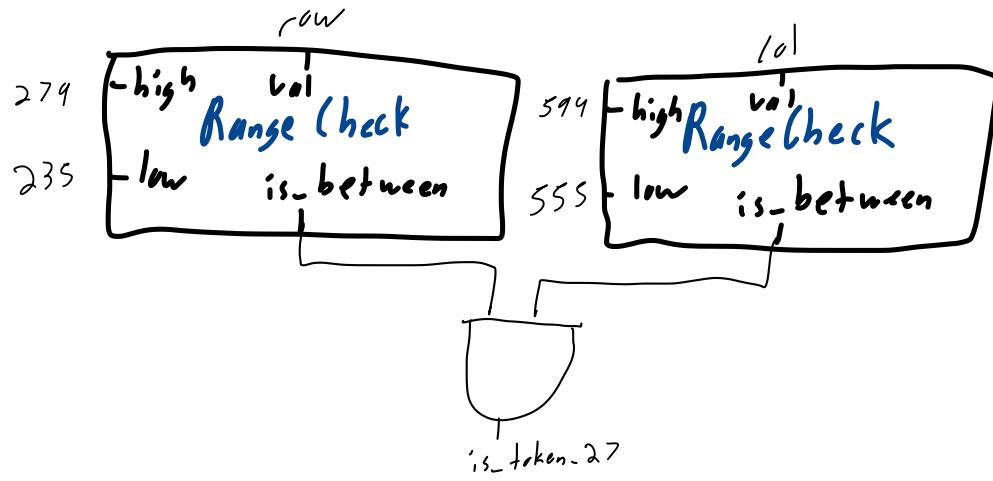


'is_token-row_3' = 'is_token_21 | is_token_22 |
'is_token_23 | is_token_24 |
'is_token_25 | 'is_token_26 |
'is_token_27


Tokens

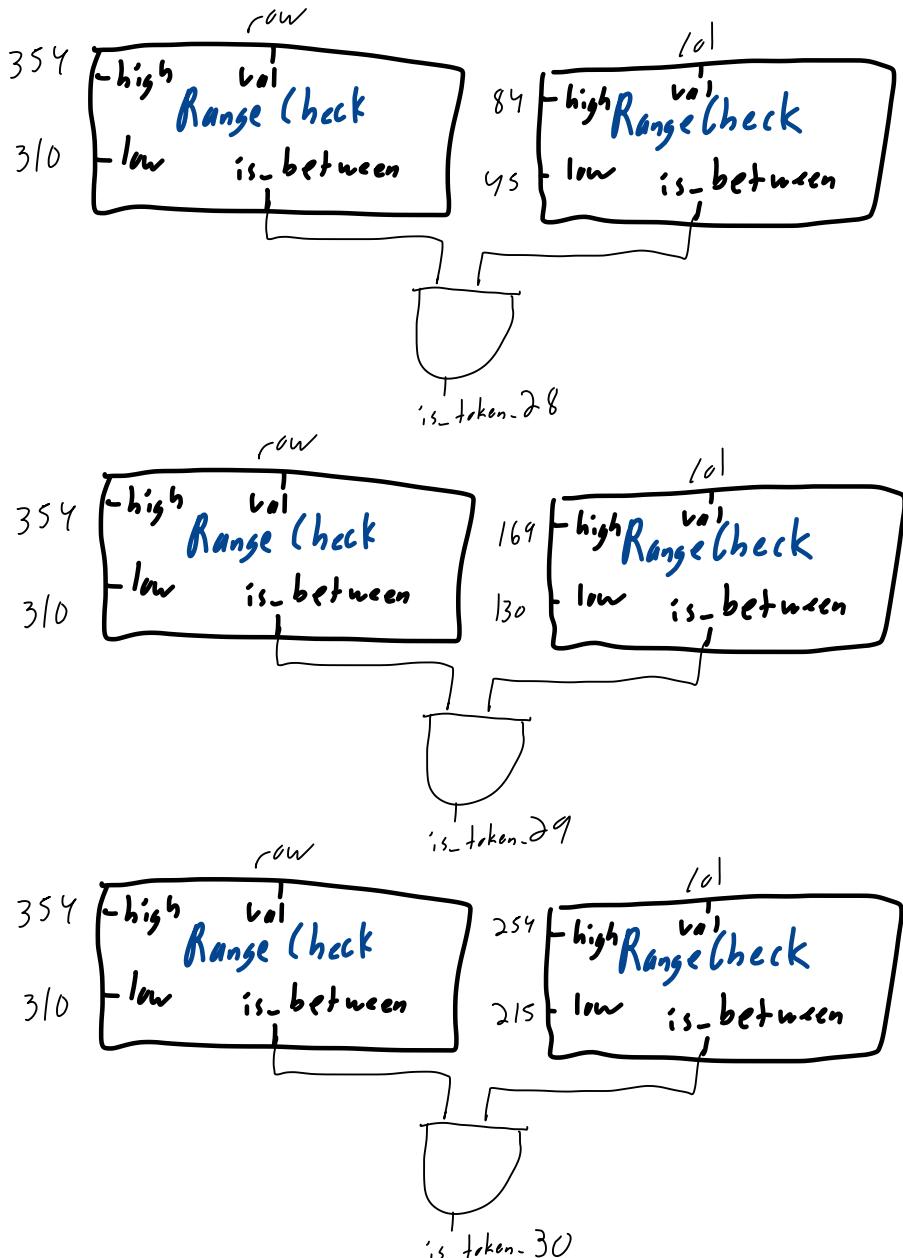

Token

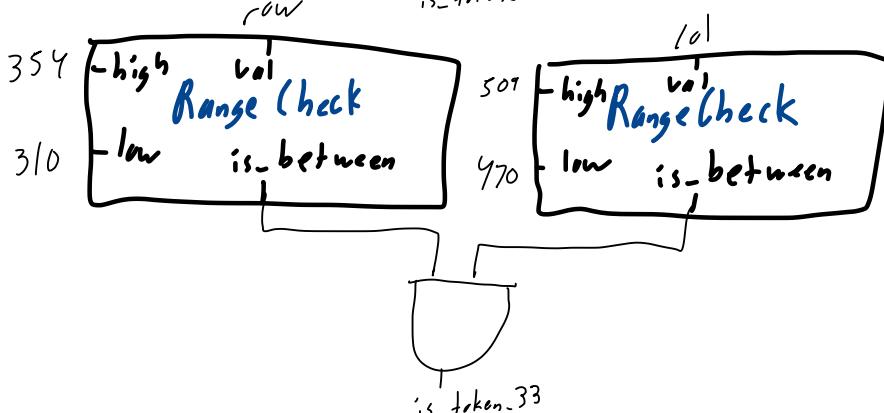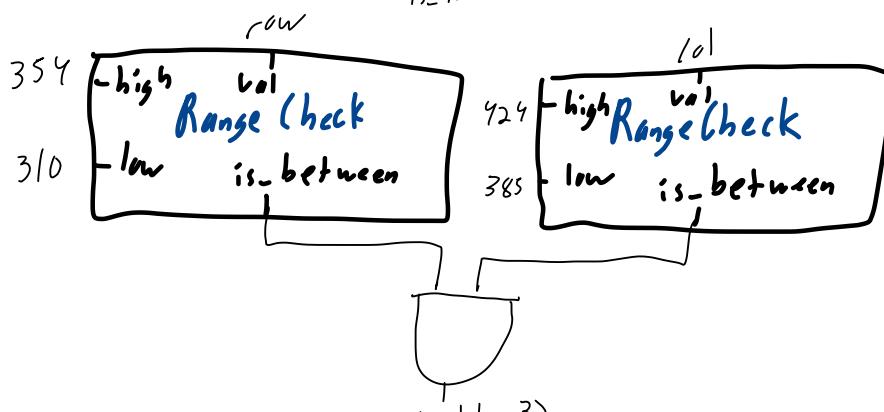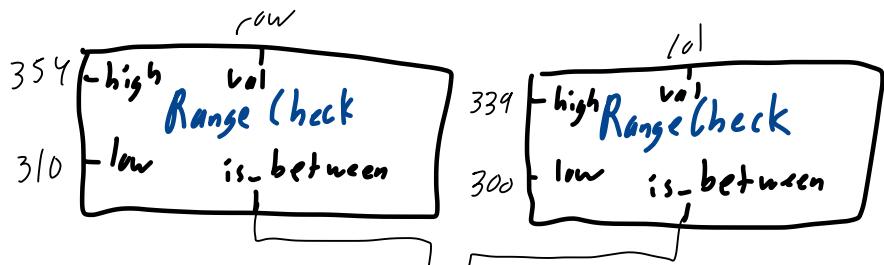


Taken



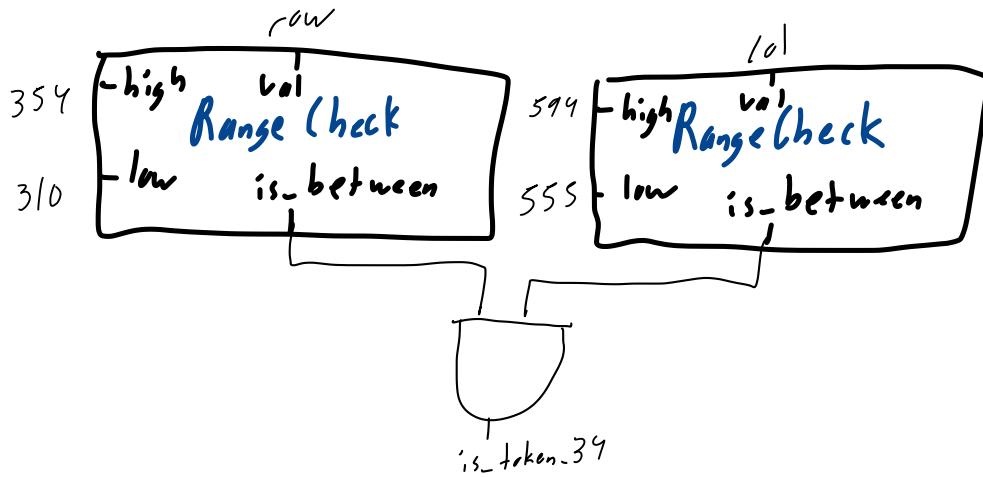


'is_taken-row-4' = 'is_taken_28 | is_taken_29 |
'is_taken_30 | is_taken_31 |
'is_taken_32 | is_taken_33 |
'is_taken_34


Token

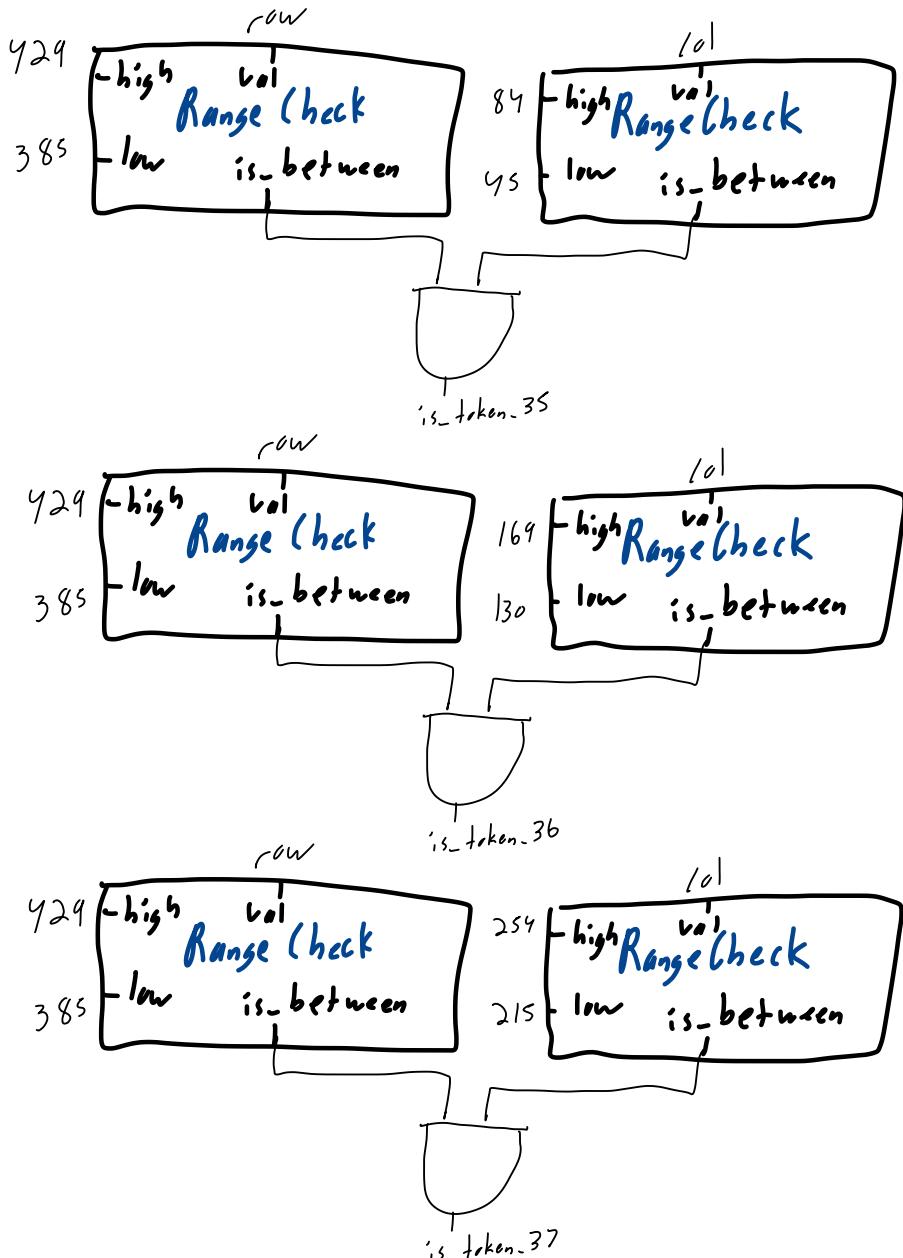

Tokens

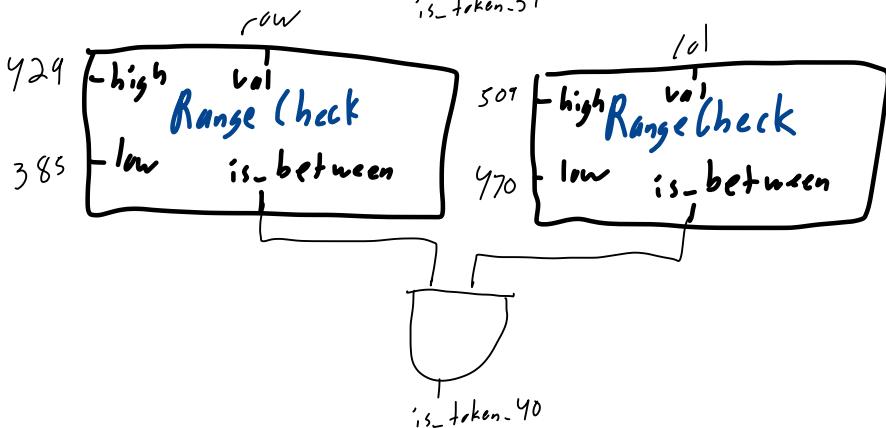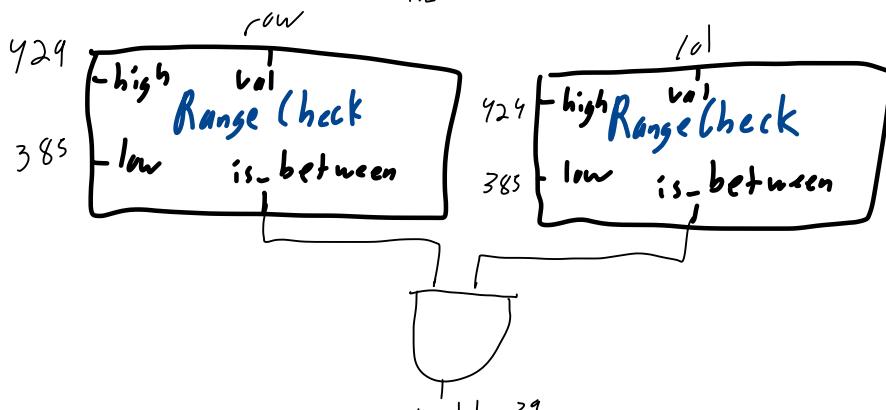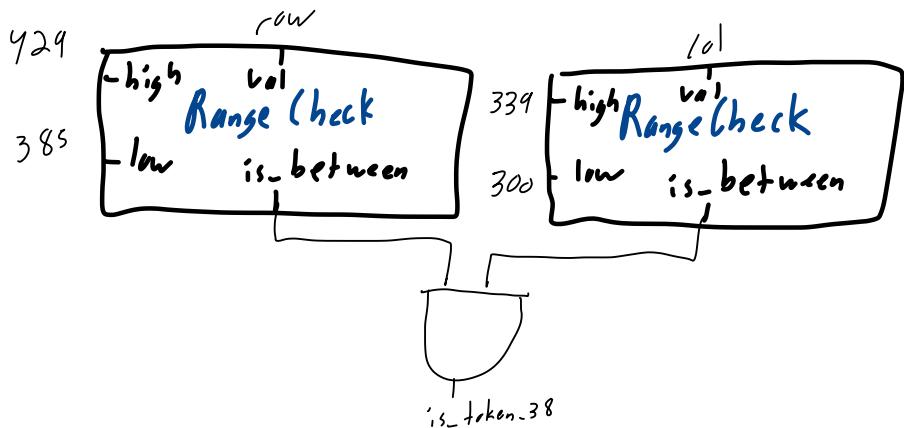

Token

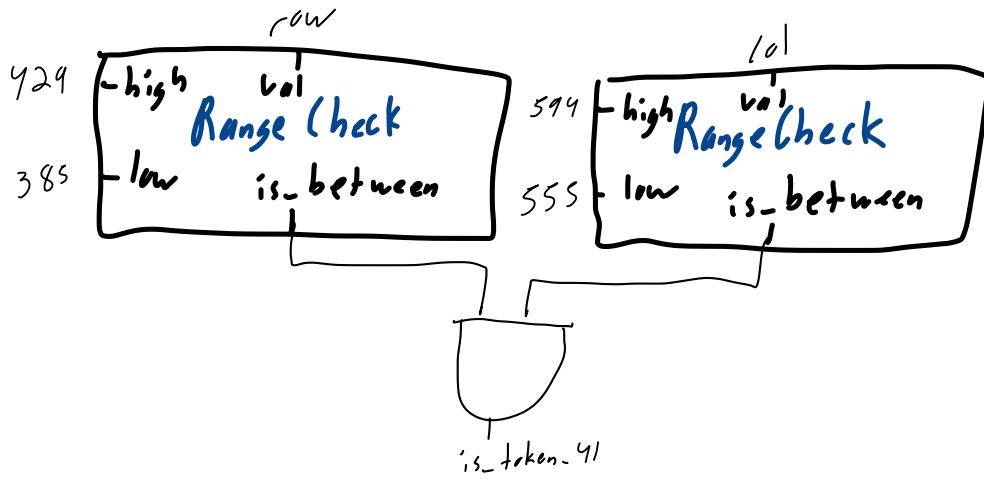


'is_token-row-5' = 'is_token_35 | is_token_36 |
 | is_token_37 | is_token_38 |
 | is_token_39 | is_token_40 |
 | is_token_41'


'is_token' = 'is_token-row-0 |
 | is_token-row-1 |
 | is_token-row-2 |
 | is_token-row-3 |
 | is_token-row-4 |
 | is_token-row-6 |

Ownership

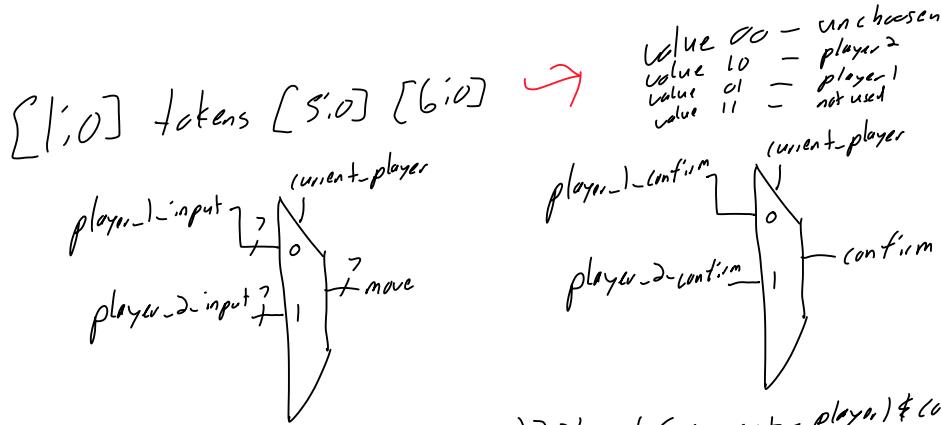Determines Ownership of each token
 Inputs [6:0] player-1-input, player-1-confirm, [6:0] player-2-input, player-2-confirm
 Outputs [1:0] tokens [5:0] [6:0]



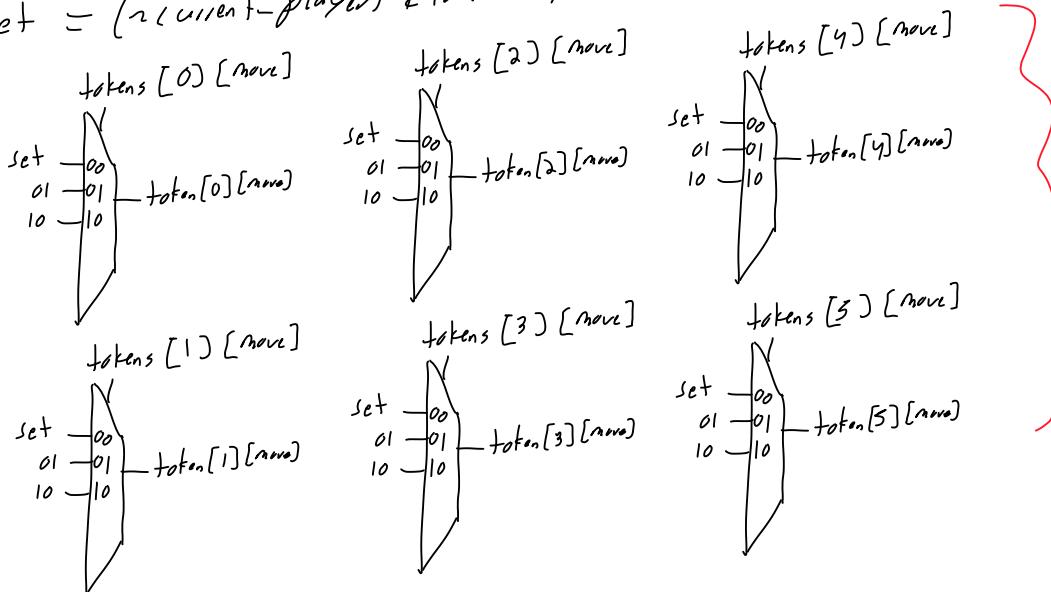
$$\text{set} = (\neg \text{current-player}) \& \text{confirm}, 2^{\prime}01 : ((\text{current-player}) \& \text{confirm}), 2^{\prime}10 ; 2^{\prime}00$$




All these are chained so the lowest is evaluated first (0, 1, 2, ...)
 and once set is assigned that is the end of the chain if else it ...

FSM win detector

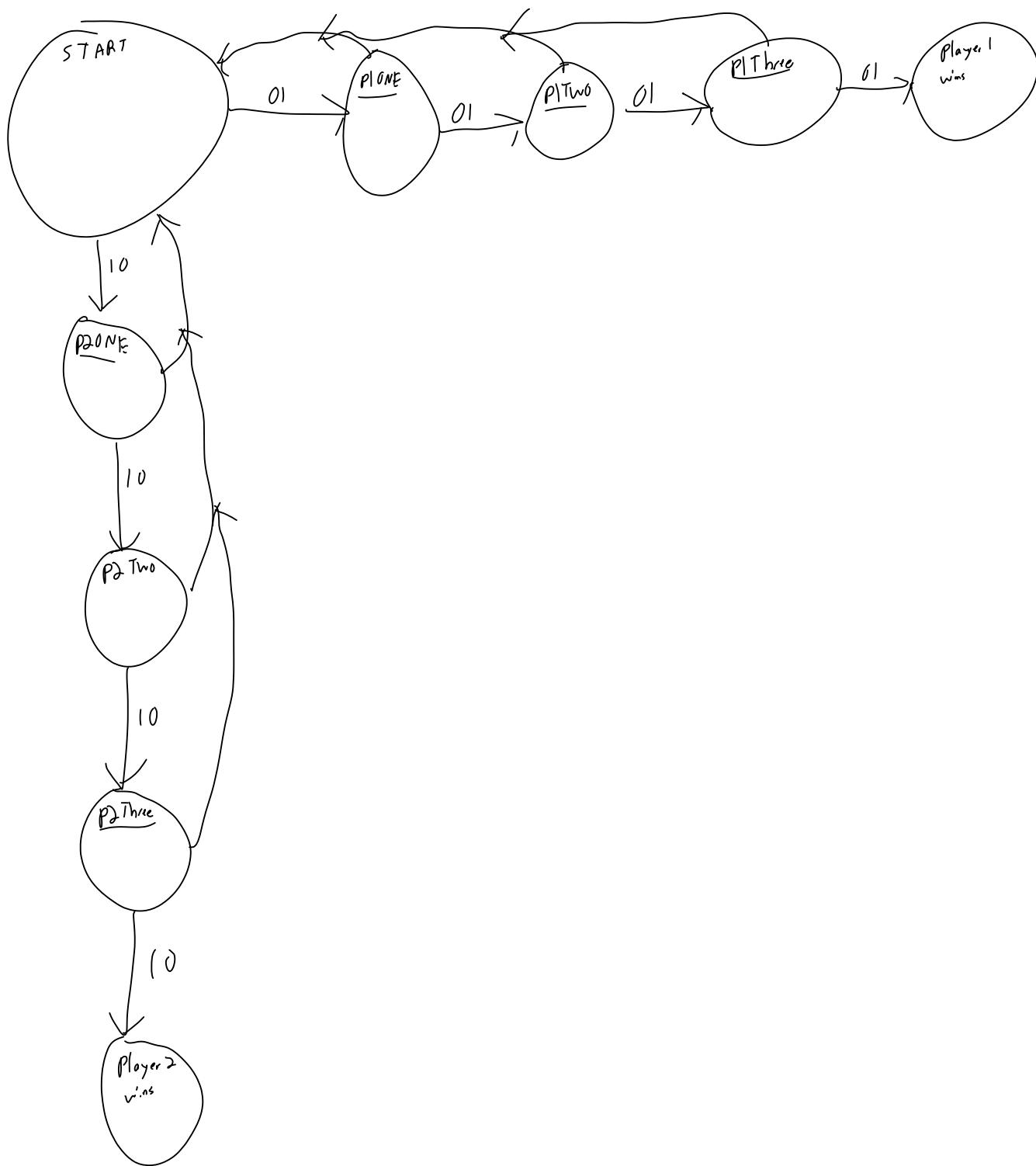

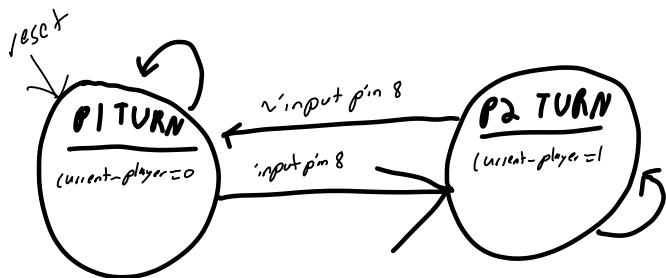FSM that determines which players turn it is




Color VGA_R, VGA_G, VGA_B

If is_board = 00, 00, 11

If is_token &
is_player_1 → = 11, 11, 00


If is_token &
is_player_2 → = 11, 00, 00

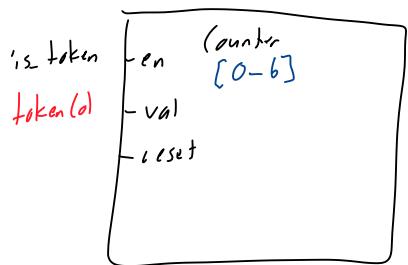If is_token &
(~is_player_1 &
~is_player_2) → 00, 00, 00



is -player_1 = (tokens[tokinRow][tokens(a)] == 2'01)? 1 : 0

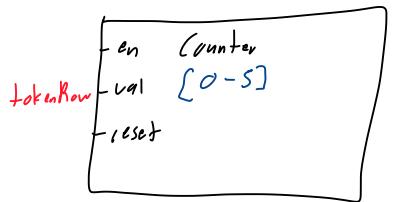
is -player_1 = (tokens[tokinRow][tokens(a)] == 2'10)? 1 : 0




PUE

This is my idea for a simplified PUE rule
Since after designing the other modules I am concerned about my
remaining area.
input col0Full, col1Full, col2Full, col3Full, col4Full, col5Full, col6Full, botTurn
outputs [6:0] bot-move, bot-confirm

as given in 18-341 L10

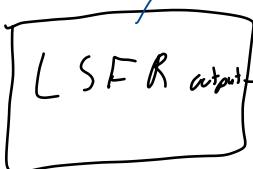


move6 = random6 & ~col6Full & botTurn

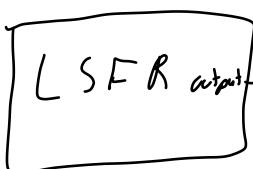


move5 = random5 & ~col5Full & botTurn




move4 = random4 & ~col4Full & botTurn

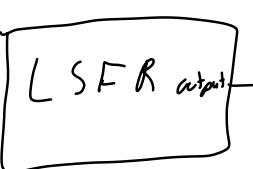

move3 = random3 & ~col3Full & botTurn

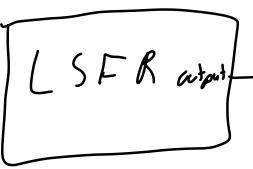

move2 = random2 & ~col2Full & botTurn

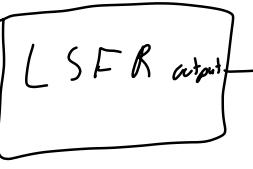

move1 = random1 & ~col1Full & botTurn




move0 = random0 & ~col0Full & botTurn

(One problem is that bot doesn't have full knowledge of the board but I am concerned about routing the 82 wires (42 tokens that need bits each) and how much area it would take to reason on them.

PVE FSM

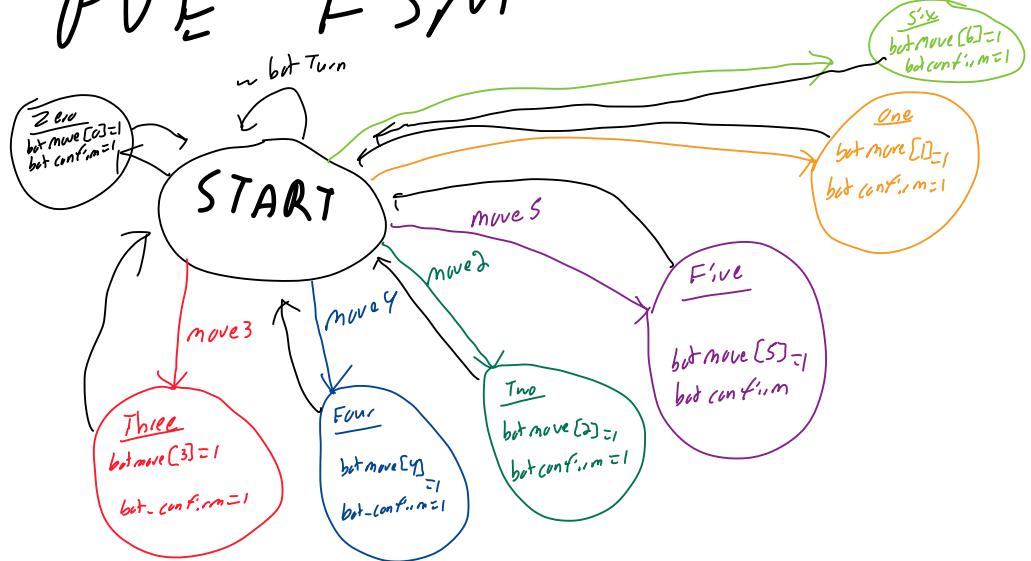- this is the order of preference for transitions since many may be possible at once



Testing

VGA can be tested using concurrent assertions to ensure that its output waveform and row/col count is correct and then tested to see if it actually outputs to a display. Board will be tested via connecting to a display and checking that the board is shown correctly. Token will be tested by forcing is_player1 and is_player2 to 1 separately and checking that all tokens are correctly shown.